

Original Input Stage – Frequency Response (Part 4)

By: branadic

DUT: WELEC W2014A, FW: 1.2.OS.091

Measurement equipment:

Signal Generator Rhode & Schwarz · 100 kHz ... 1000 MHz · SMG, Oscilloscope TDS5104B

As known, the frequency response of the original stage shows some kind of peaking with maximum at about 140MHz. The x axis shows the frequency and y axis is normalized to 0 dB.

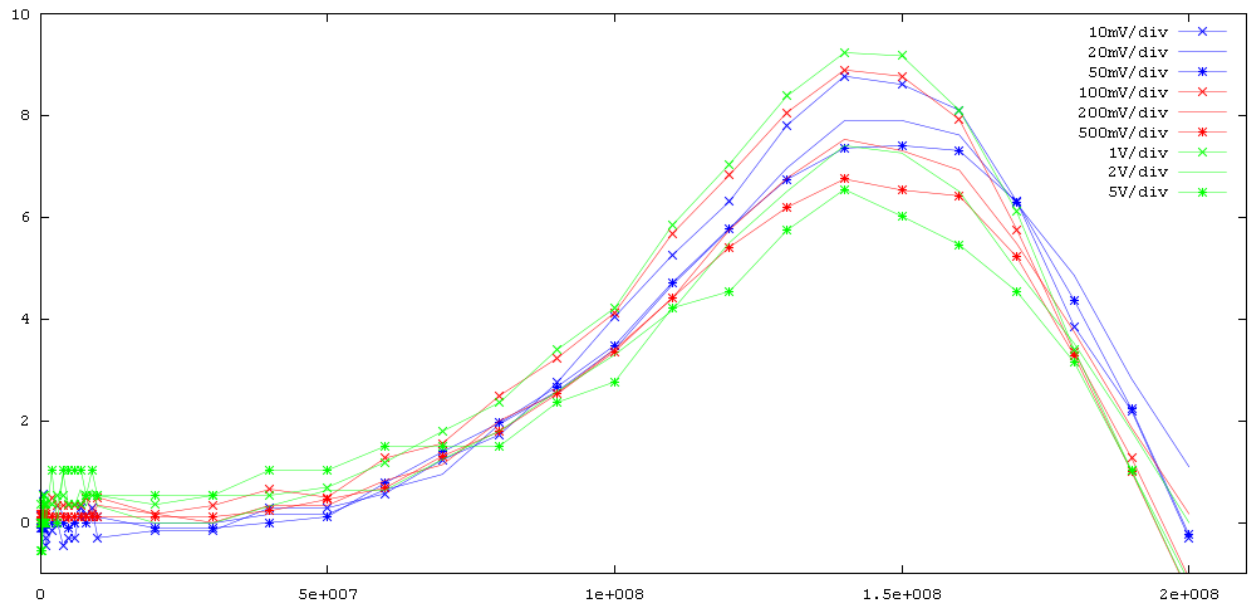


Abbildung 1: Frequency Response of original stage in linear plot

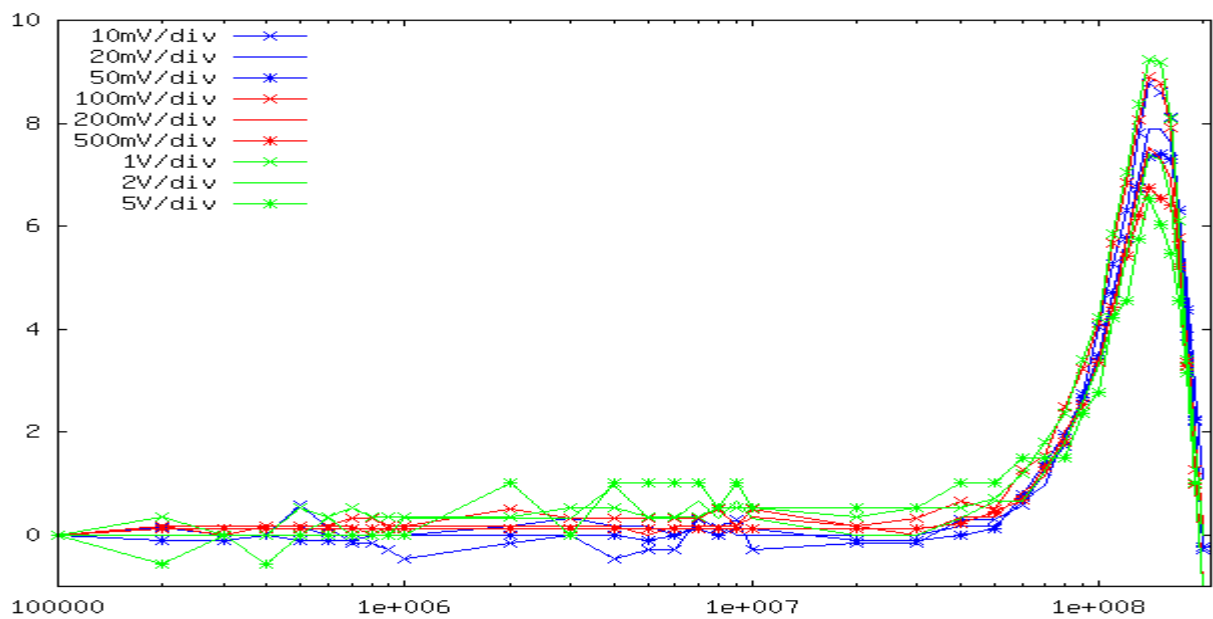


Abbildung 2: Frequency Response of original stage in log plot

It's also known, that there are $0\ \Omega$ resistors between the last opamp (AD8131) and the ADC's (4x MAX1121).

In the following measurements this both resistors were replaced by $24.9\ \Omega$ and frequency response was detected again.

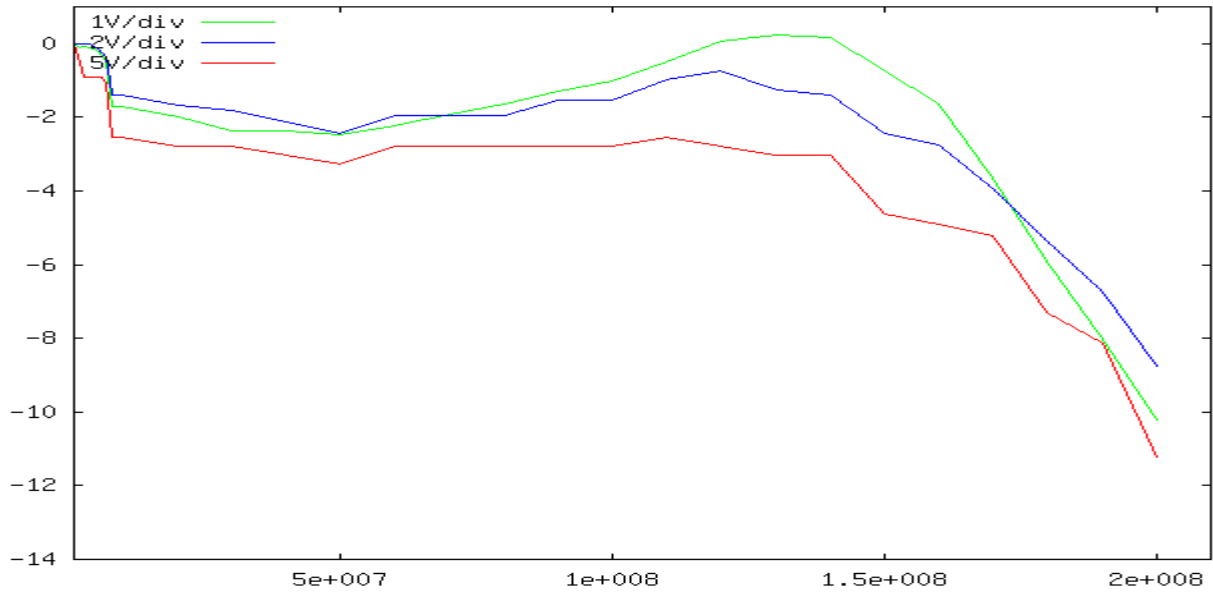


Abbildung 3: Frequency Response of the modified stage in linear plot

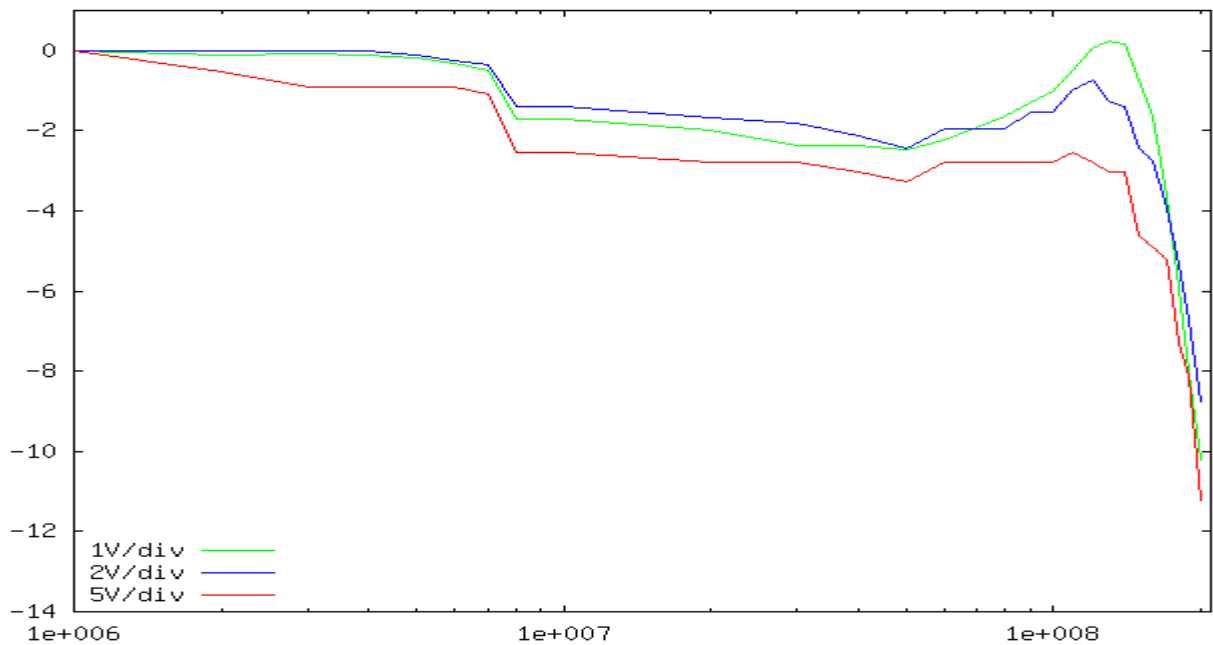


Abbildung 4: Frequency Response of modified stage in log plot

It can be seen, that peaking has decreased, but there is a break-in of nearly -2 dB between 7 MHz and 8 MHz. The value and the function of the resistors is not perfect, influencing the amplitude in the whole frequency range.

A better approach is to set U12 to a fixed output impedance i.e. $50\ \Omega$ in each path and connect a LC filter circuit with $100\ \Omega$ input impedance and about 4th order. A resistor in parallel to the ADCs reduces the resulting resistor ($1.1\ \text{k}\Omega \parallel R$). The filter needs to transform the input impedance to the output impedance.

It could also be possible, to use the parasitic capacitance of the ADCs as a part of the filter. Therefore the filter structure could be a Butterworth filter in low pass T configuration.

This action could steady frequency behaviour and reduce noise, which needs to be proved.

branadic